

## Section 8-2 and 8-3: Average and Complex Power

**Problem 8.9** Determine the complex power, apparent power, average power absorbed, reactive power, and power factor (including whether it is leading or lagging) for a load circuit whose voltage and current at its input terminals are given by:

- (a)  $v(t) = 100 \cos(377t - 30^\circ)$  V,  
 $i(t) = 2.5 \cos(377t - 60^\circ)$  A.
- (b)  $v(t) = 25 \cos(2\pi \times 10^3 t + 40^\circ)$  V,  
 $i(t) = 0.2 \cos(2\pi \times 10^3 t - 10^\circ)$  A.
- (c)  $\mathbf{V}_{\text{rms}} = 110 \angle 60^\circ$  V,  $\mathbf{I}_{\text{rms}} = 3 \angle 45^\circ$  A.
- (d)  $\mathbf{V}_{\text{rms}} = 440 \angle 0^\circ$  V,  $\mathbf{I}_{\text{rms}} = 0.5 \angle 75^\circ$  A.
- (e)  $\mathbf{V}_{\text{rms}} = 12 \angle 60^\circ$  V,  $\mathbf{I}_{\text{rms}} = 2 \angle -30^\circ$  A.

**Solution:**

(a)

$$\mathbf{V}_{\text{rms}} = \frac{100}{\sqrt{2}} e^{-j30^\circ} \text{ V},$$

$$\mathbf{I}_{\text{rms}} = \frac{2.5}{\sqrt{2}} e^{-j60^\circ} \text{ A}.$$

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \frac{100}{\sqrt{2}} e^{-j30^\circ} \times \frac{2.5}{\sqrt{2}} e^{j60^\circ} = 125 e^{j30^\circ} \quad (\text{VA})$$

$$S = |\mathbf{S}| = 125 \text{ VA}$$

$$P_{\text{av}} = \Re\{\mathbf{S}\} = 125 \cos 30^\circ = 108.25 \text{ W}$$

$$Q = \Im\{\mathbf{S}\} = 125 \sin 30^\circ = 62.5 \text{ VAR}$$

$$\phi_s = \phi_v - \phi_i = -30^\circ + 60^\circ = 30^\circ \quad (\text{hence } pf \text{ is lagging})$$

$$pf = \cos 30^\circ = 0.866.$$

(b)

$$\mathbf{V}_{\text{rms}} = \frac{25}{\sqrt{2}} e^{j40^\circ} \text{ V},$$

$$\mathbf{I}_{\text{rms}} = \frac{0.2}{\sqrt{2}} e^{-j10^\circ} \text{ A},$$

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 2.5 e^{j50^\circ} \quad (\text{VA}),$$

$$S = 2.5 \text{ VA}, \quad \phi_s = 50^\circ \text{ (lagging)}$$

$$P_{\text{av}} = 2.5 \cos 50^\circ = 1.61 \text{ W},$$

$$Q = 2.5 \sin 50^\circ = 1.92 \text{ VAR},$$

$$pf = \cos 50^\circ = 0.64 \text{ lagging}.$$

(c)

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 110 e^{j60^\circ} \times 3 e^{-j45^\circ} = 330 e^{j15^\circ} \text{ VA}.$$

$$S = 330 \text{ VA},$$

$$\begin{aligned}P_{\text{av}} &= 330 \cos 15^\circ = 318.76 \text{ W}, \\Q &= 330 \sin 15^\circ = 85.41 \text{ VAR}, \\pf &= \cos 15^\circ = 0.97 \text{ (lagging)}.\end{aligned}$$


(d)

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 440 \times 0.5 e^{-j75^\circ} = 220 e^{-j75^\circ} \text{ VA}, \\S &= 220 \text{ VA}, \\P_{\text{av}} &= 220 \cos(-75^\circ) = 56.94 \text{ W}, \\Q &= 220 \sin(-75^\circ) = -212.50 \text{ VAR}, \\pf &= \cos(-75^\circ) = 0.26 \text{ (leading)}.\end{aligned}$$

(e)


$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 12 e^{j60^\circ} \times 2 e^{j30^\circ} = 24 e^{j90^\circ} \text{ VA}, \\S &= 24 \text{ VA}, \\P_{\text{av}} &= 24 \cos 90^\circ = 0, \\Q &= 24 \sin 90^\circ = 24 \text{ VAR}, \\pf &= \cos 90^\circ = 0 \text{ (purely inductive with } \mathbf{I} \text{ lagging } \mathbf{V} \text{ by } 90^\circ)\end{aligned}$$

**Problem 8.11** In the circuit of Fig. P8.11,  $i_s(t) = 0.2 \sin 10^5 t$  A,  $R = 20 \Omega$ ,  $L = 0.1$  mH, and  $C = 2 \mu\text{F}$ . Show that the sum of the complex powers for the three passive elements is equal to the complex power of the source.

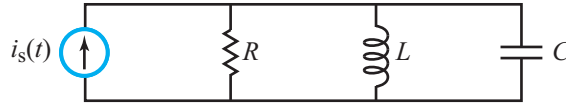

**Figure P8.11:** Circuit for Problem 8.11.

**Solution:**

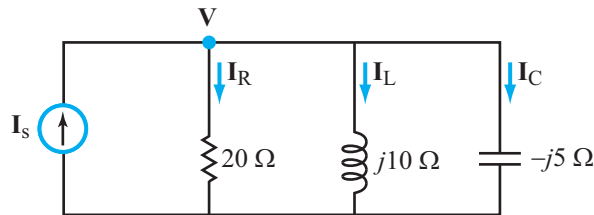

$$\mathbf{I}_s = 0.2 \angle 0^\circ \text{ A}$$

$$\mathbf{Z}_L = j\omega L = j10^5 \times 10^{-4} = j10 \Omega$$

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{10^5 \times 2 \times 10^{-6}} = -j5 \Omega.$$

$$\frac{\mathbf{V}}{20} + \frac{\mathbf{V}}{j10} + \frac{\mathbf{V}}{-j5} = \mathbf{I}_s = 0.2$$

$$\mathbf{V} = 1.79e^{-j63.4^\circ} \text{ V.}$$

$$\mathbf{I}_R = \frac{\mathbf{V}}{20} = \frac{1.79e^{-j63.4^\circ}}{20} \text{ A.}$$

$$\mathbf{S}_R = \frac{1}{2} \mathbf{V} \mathbf{I}_R^* = \frac{(1.79)^2}{2 \times 20} = 0.08 \text{ VA.}$$

$$\mathbf{I}_L = \frac{\mathbf{V}}{j10} = \frac{1.79}{10} e^{-j153.4^\circ}$$

$$\mathbf{S}_L = \frac{1}{2} \mathbf{V} \mathbf{I}_L^* = \frac{1.79}{2} e^{-j63.4^\circ} \times \frac{1.79}{10} e^{j153.4^\circ} = 0.16e^{j90^\circ} = 0 + j0.16 \text{ VA.}$$

$$\mathbf{I}_C = \frac{\mathbf{V}}{-j5} = \frac{1.79}{5} e^{j26.6^\circ} \text{ A.}$$

$$\mathbf{S}_C = \frac{1}{2} \mathbf{V} \mathbf{I}_C^* = \frac{1}{2} 1.79e^{-j63.4^\circ} \times \frac{1.79}{5} e^{-j26.6^\circ} = 0.32e^{-j90^\circ} = 0 - j0.32 \text{ VA.}$$

$$\mathbf{S}_T = \mathbf{S}_R + \mathbf{S}_L + \mathbf{S}_C = 0.08 + j0.16 - j0.32 = 0.08 - j0.16 \text{ VA.}$$

For the source,


$$\mathbf{S}_s = \frac{1}{2} \mathbf{V} \mathbf{I}_s^* = \frac{1}{2} 1.79e^{-j63.4^\circ} \times 0.2 = 0.179e^{-j63.4^\circ}$$

$$\begin{aligned} &= 0.179 \cos 63.4^\circ - j0.179 \sin 63.4^\circ \\ &= 0.08 - j0.16 \text{ VA.} \end{aligned}$$


Hence

$$\mathbf{S}_T = \mathbf{S}_s.$$

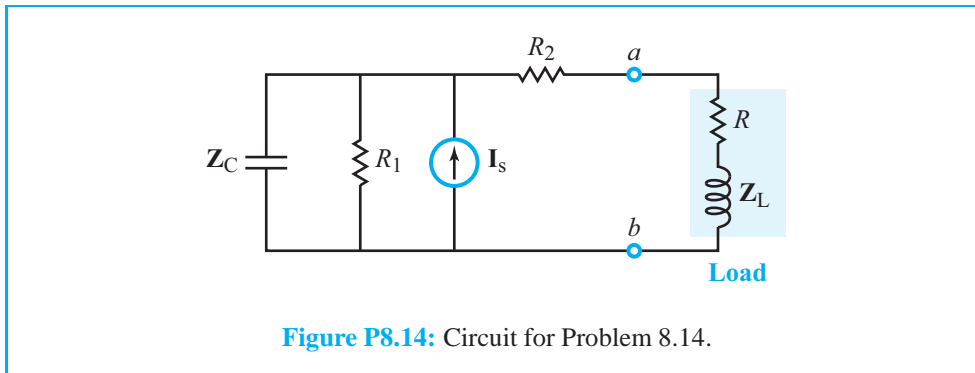**Problem 8.14** Determine  $\mathbf{S}$  for the RL load in the circuit of Fig. P8.14, given that  $\mathbf{I}_s = 4\angle 0^\circ$  A,  $R_1 = 10\ \Omega$ ,  $R_2 = 5\ \Omega$ ,  $\mathbf{Z}_C = -j20\ \Omega$ ,  $R = 10\ \Omega$ , and  $\mathbf{Z}_L = j20\ \Omega$ .



**Solution:**

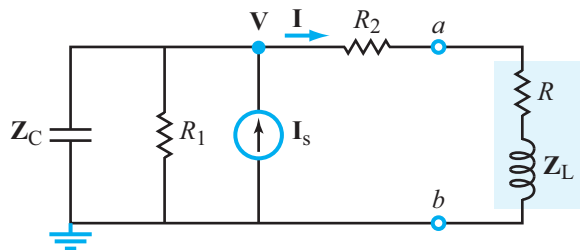

$$\mathbf{V} \left( \frac{1}{\mathbf{Z}_C} + \frac{1}{R_1} + \frac{1}{R_2 + R + \mathbf{Z}_L} \right) = \mathbf{I}_s$$

$$\mathbf{V} \left( \frac{1}{-j20} + \frac{1}{10} + \frac{1}{5 + 10 + j20} \right) = 4$$

Solution gives

$$\mathbf{V} = 31.6 - j4.6 = 31.93e^{-j8.28^\circ} \text{ V.}$$

For RL load:

$$\begin{aligned} \mathbf{S} &= \frac{1}{2} \mathbf{V}_{ab} \mathbf{I}^* \\ &= \frac{1}{2} \frac{(10 + j20)}{15 + j20} \mathbf{V} \times \left( \frac{\mathbf{V}}{15 + j20} \right)^* \\ &= (5 + j10) \frac{|\mathbf{V}|^2}{|15 + j20|^2} = 11.18e^{j63.4^\circ} \times \frac{(31.93)^2}{625} = 18.24e^{j63.4^\circ} \text{ VA.} \end{aligned}$$

**Problem 8.20** The apparent power entering a certain load  $\mathbf{Z}$  is 250 VA at a power factor of 0.8 leading. If the rms phasor voltage of the source is 125 V at 1 MHz:

- (a) Determine  $\mathbf{I}_{\text{rms}}$  going into the load
- (b) Determine  $\mathbf{S}$  into the load
- (c) Determine  $\mathbf{Z}$
- (d) The equivalent impedance of the load circuit should be of the form  $\mathbf{Z} = R + j\omega L$  or  $\mathbf{Z} = R - j/\omega C$ . Determine the value of  $L$  or  $C$ , whichever is applicable.

**Solution:**

(a) From

$$S = V_{\text{rms}} I_{\text{rms}},$$

$$I_{\text{rms}} = \frac{S}{V_{\text{rms}}} = \frac{250}{125} = 2 \text{ A.}$$

(b)  $pf = 0.8$  leading means  $\phi_z$  is negative. Hence,

$$\phi_z = -\cos^{-1} 0.8 = -36.87^\circ.$$

$$\mathbf{S} = S \cos \phi_z + jS \sin \phi_z$$

$$= 250[\cos(-36.87^\circ) + j \sin(-36.87^\circ)] = (200 - j150) \text{ VA.}$$

(c)

$$P_{\text{av}} = I_{\text{rms}}^2 R$$

$$R = \frac{P_{\text{av}}}{I_{\text{rms}}^2} = \frac{200}{4} = 50 \ \Omega.$$

Also,

$$Q = I_{\text{rms}}^2 X$$

$$X = \frac{Q}{I_{\text{rms}}^2} = \frac{-150}{4} = -37.5 \ \Omega.$$

Hence,


$$\mathbf{Z} = R + jX = (50 - j37.5) \ \Omega.$$

(d)  $\frac{-j}{\omega C} = -j37.5$ , or

$$C = \frac{1}{37.5\omega} = \frac{1}{37.5 \times 2\pi \times 10^6} = 4.24 \text{ nF.}$$

## Section 8-4: Power Factor

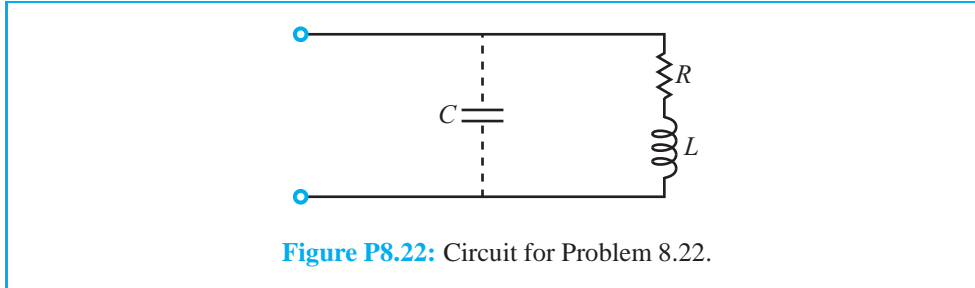**Problem 8.22** The RL load in Fig. P8.22 is compensated by adding the shunt capacitance  $C$  so that the power factor of the combined (compensated) circuit is exactly unity. How is  $C$  related to  $R$ ,  $L$ , and  $\omega$  in that case?



**Solution:** For the combined load, the impedance is

$$\begin{aligned} Z &= (R + j\omega L) \parallel \left( \frac{1}{j\omega C} \right) \\ &= \frac{(R + j\omega L) \left( \frac{-j}{\omega C} \right)}{R + j \left( \omega L - \frac{1}{\omega C} \right)} \\ &= \frac{\omega L - jR}{\omega RC - j(1 - \omega^2 LC)} \\ &= \frac{(\omega L - jR)[\omega RC + j(1 - \omega^2 LC)]}{[\omega RC - j(1 - \omega^2 LC)][\omega RC + j(1 - \omega^2 LC)]} \\ &= \frac{[\omega^2 RLC + R(1 - \omega^2 LC)]}{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2} + \frac{j[\omega L(1 - \omega^2 LC) - \omega R^2 C]}{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2} \end{aligned}$$


For the  $pf$  to be unity, the imaginary component of  $Z$  has to be zero, which is realized if

$$\omega L(1 - \omega^2 LC) - \omega R^2 C = 0.$$

or

$$C = \frac{L}{R^2 + \omega^2 L^2}.$$

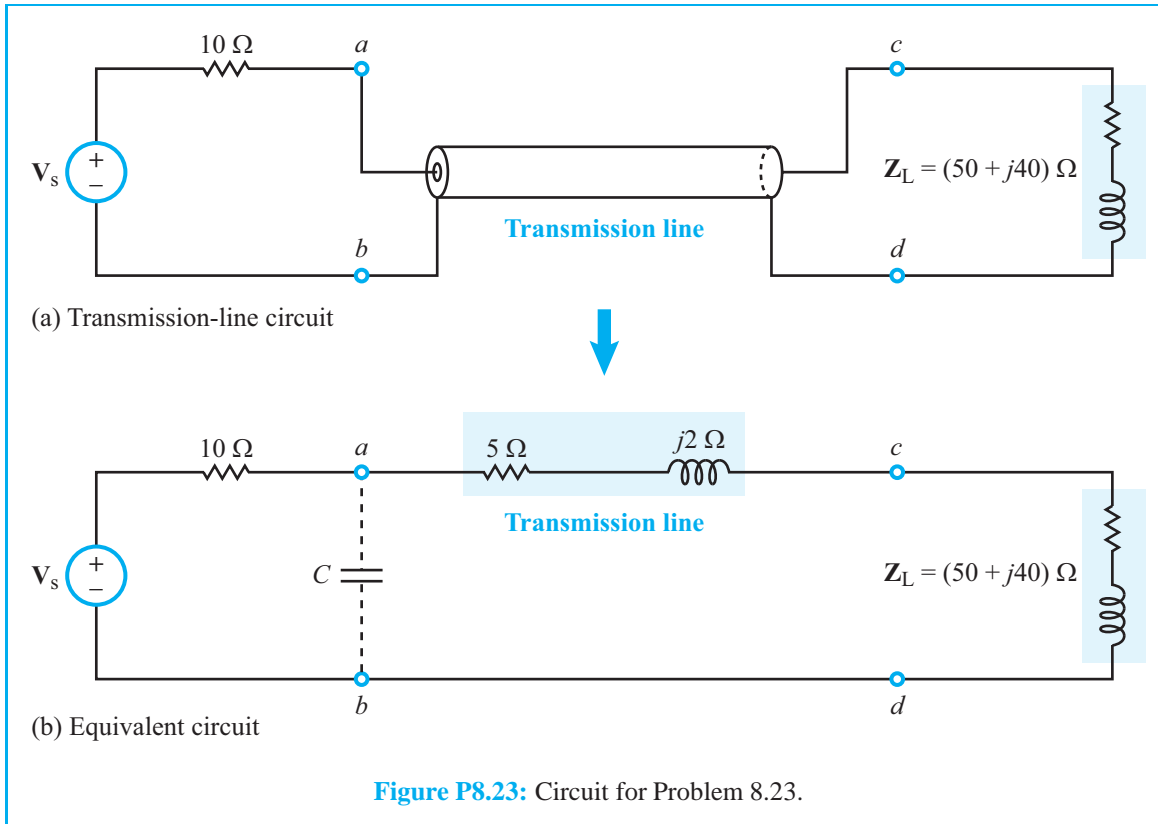**Problem 8.23** The generator circuit shown in Fig. P8.23 is connected to a distant load via a long coaxial transmission line. The overall circuit can be modeled as in Fig. P8.23(b), in which the transmission line is represented by an equivalent impedance  $\mathbf{Z}_{\text{line}} = (5 + j2) \Omega$ .



- (a) Determine the power factor of voltage source  $\mathbf{V}_s$ .
- (b) Specify the capacitance of a shunt capacitor  $C$  that would raise the power factor of the source to unity when connected between terminals  $(a, b)$ . The source frequency is 1.5 kHz.

**Solution:**

(a) The power factor of the source is the same as the phase of the impedance representing the entire circuit connected to  $\mathbf{V}_s$ . Thus,

$$\mathbf{Z}_T = 10 + (5 + j2) + (50 + j40) = (65 + j42) \Omega,$$

$$\phi_Z = \tan^{-1} \frac{42}{65} = 32.87^\circ,$$

$$pf = \cos \phi_Z = 0.84, \text{ lagging.}$$

(b) For the circuit to the right of terminals  $(a, b)$ , the impedance—with a shunt capacitance  $C$ —is:

$$\begin{aligned} \mathbf{Z}_{ab} &= \left( \frac{-j}{\omega C} \right) \parallel (55 + j42) \\ &= \frac{-jX_C(55 + j42)}{55 + j(42 - X_C)} \end{aligned}$$



where  $X_C = \frac{1}{\omega C}$ .  
Simplifying,

$$\begin{aligned} \mathbf{Z}_{ab} &= \frac{42X_C - j55X_C}{55^2 + (42 - X_C)^2} \cdot [55 - j(42 - X_C)] \\ &= \frac{[42 \times 55X_C - 55X_C(42 - X_C)] - j[55^2X_C + 42X_C(42 - X_C)]}{3025 + (42 - X_C)^2} \end{aligned}$$

For a *pf* of 1, the imaginary part of  $\mathbf{Z}_{ab}$  should be zero,

$$55^2X_C + 42X_C(42 - X_C) = 0.$$

Solution gives


$$X_C = 114.02,$$

or


$$C = \frac{1}{\omega X_C} = \frac{1}{2\pi \times 1.5 \times 10^3 \times 114.02} = 930.5 \text{ nF}.$$

**Problem 8.25** Use the power information given for the circuit in Fig. P8.25 to determine:

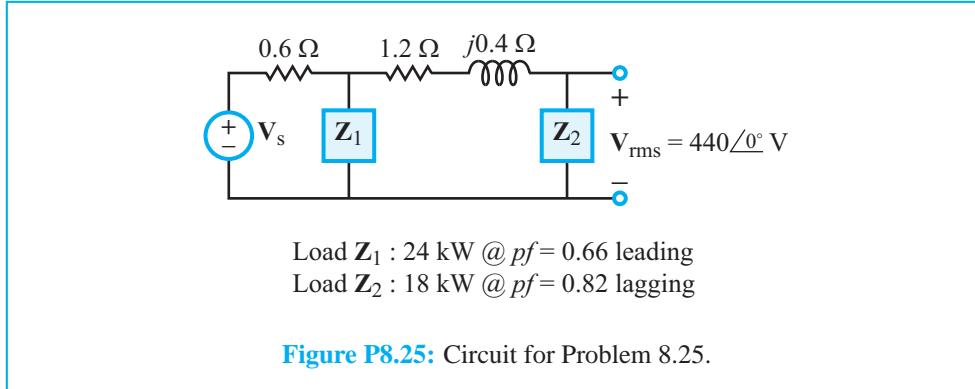- (a)  $Z_1$  and  $Z_2$
- (b) the rms value of  $V_s$ .



**Solution:**

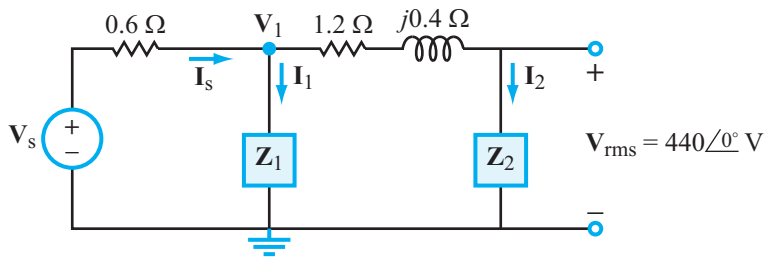

(a) For load  $Z_2$ :

$$\phi_{Z_2} = \cos^{-1} 0.82 = 34.9^\circ.$$

Since  $\phi_{Z_2} = \phi_{v_2} - \phi_{i_2}$ , and  $\phi_{v_2} = 0$ ,  $\implies \phi_{i_2} = -34.9^\circ$ .

$$P_{av_2} = V_{rms} I_{2,rms} \cos \phi_{Z_2}$$

$$18 \times 10^3 = 440 I_{2,rms} \cos 34.9^\circ,$$

or

$$I_{2,rms} = 49.88 \text{ A},$$

and

$$S_2 = V_{rms} I_{2,rms} = 440 \times 49.88 = 21.95 \text{ kVA}.$$

Also,  $I_{2,rms} = 49.88 \angle -34.9^\circ \text{ A}$ .

If  $Z_2 = R_2 + jX_2$ ,

$$P_{av_2} = I_{2,rms}^2 R_2 \implies R_2 = \frac{18 \times 10^3}{(49.88)^2} = 7.23 \Omega$$

$$Q_2 = S_2 \sin \phi_{Z_2} = 21.95 \times 10^3 \sin 34.9^\circ = 12.56 \text{ kVAR}$$

But

$$Q_2 = I_{2,rms}^2 X_2 \implies X_2 = \frac{12.56 \times 10^3}{(49.88)^2} = 5.05 \Omega.$$

Hence,

$$\mathbf{Z}_2 = (7.23 + j5.05) \Omega.$$

To determine  $\mathbf{Z}_1$ , we first determine the voltage across it,  $\mathbf{V}_{1\text{rms}}$ :

$$\begin{aligned}\mathbf{V}_{1\text{rms}} &= (1.2 + j0.4 + \mathbf{Z}_2)\mathbf{I}_{2\text{rms}} \\ &= (1.2 + j0.4 + 7.23 + j5.05)49.88e^{-j34.9^\circ} \\ &= 500.8\angle-2^\circ \text{ V.}\end{aligned}$$

For load  $\mathbf{Z}_1$ :

$$\begin{aligned}\phi_{Z_1} &= -\cos^{-1} 0.66 = -48.7^\circ \\ S_1 &= \frac{P_{\text{av}1}}{\cos \phi_{Z_1}} = \frac{24}{0.66} = 36.36 \text{ kVA} \\ I_{1\text{rms}} &= \frac{S_1}{V_{1\text{rms}}} = \frac{36.36 \times 10^3}{500.8} = 72.6 \text{ A} \\ \phi_{Z_1} &= \phi_{v_1} - \phi_{i_1} \\ -48.7^\circ &= -2 - \phi_{i_1} \implies \phi_{i_1} = 46.7^\circ. \\ \mathbf{I}_{1\text{rms}} &= 72.6\angle 46.7^\circ \text{ A.} \\ P_{\text{av}1} &= \mathbf{I}_{1\text{rms}}^2 R_1 \implies R_1 = \frac{24 \times 10^3}{(72.6)^2} = 4.55 \Omega \\ Q_1 &= S_1 \sin \phi_{Z_1} = 36.36 \times 10^3 \sin(-48.7^\circ) = -27.32 \text{ kVAR} \\ X_1 &= \frac{Q_1}{I_{1\text{rms}}^2} = \frac{-27.32 \times 10^3}{(72.6)^2} = -5.18 \Omega\end{aligned}$$

Hence,

$$\mathbf{Z}_1 = (4.55 - j5.18) \Omega.$$

**(b)** Given  $\mathbf{I}_1$  and  $\mathbf{I}_2$ , we can now determine  $\mathbf{I}_s$ :

$$\begin{aligned}\mathbf{I}_{s\text{rms}} &= \mathbf{I}_{1\text{rms}} + \mathbf{I}_{2\text{rms}} \\ &= 72.6e^{j46.7^\circ} + 49.88e^{-j34.9^\circ} \\ &= (90.7 + j24.3) \text{ A} \\ \mathbf{V}_{s\text{rms}} &= \mathbf{V}_{1\text{rms}} + 0.6\mathbf{I}_{s\text{rms}} \\ &= 500.8e^{-j2^\circ} + 0.6(90.7 + j24.3) = (554.9 - j2.9) \text{ V.}\end{aligned}$$

**Problem 8.27** For the circuit in Fig. P8.27, choose the load impedance  $\mathbf{Z}_L$  so that the power dissipated in it is a maximum. How much power will that be?


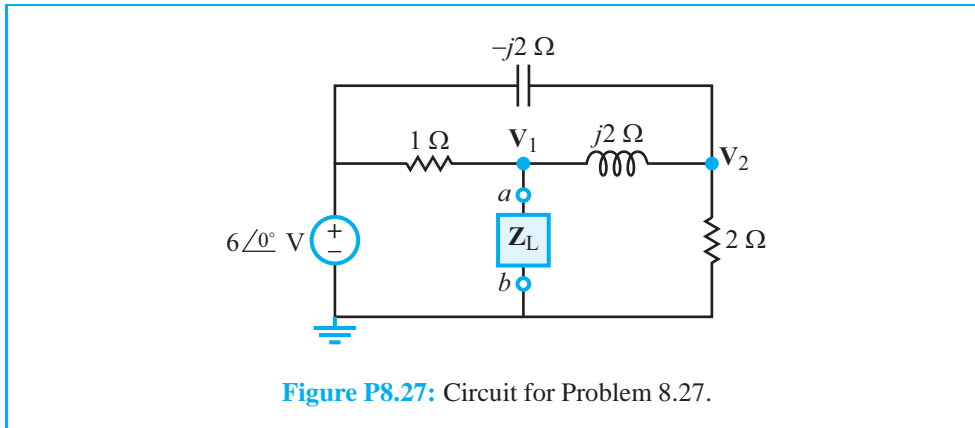


Figure P8.27: Circuit for Problem 8.27.

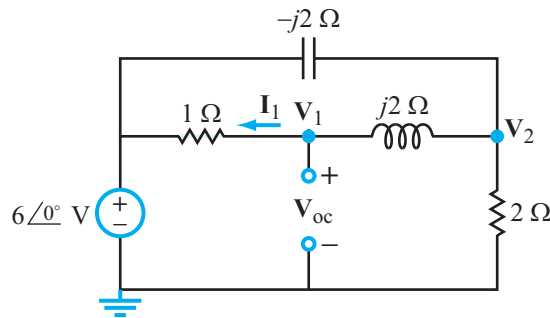**Solution:** To determine  $\mathbf{V}_s$  of the equivalent source circuit, we remove  $\mathbf{Z}_L$  and calculate  $\mathbf{V}_{oc}$  at terminals  $(a, b)$ .



At node  $\mathbf{V}_2$ :

$$\frac{\mathbf{V}_2 - 6}{-j2} + \frac{\mathbf{V}_2}{2} + \frac{\mathbf{V}_2 - 6}{1 + j2} = 0 \quad \Rightarrow \quad \mathbf{V}_2 = 0.6(3 + j) \text{ V.}$$

$$\mathbf{I}_1 = \frac{\mathbf{V}_2 - 6}{1 + j2} = \frac{\mathbf{V}_1 - 6}{1}$$

Hence,

$$\mathbf{V}_s = \mathbf{V}_1 = \frac{\mathbf{V}_2 - 6}{1 + j2} + 6 = \frac{0.6(3 + j) - 6}{1 + j2} + 6 = 5.7 \angle 18.4^\circ \text{ V.}$$

To determine  $\mathbf{Z}_{Th}$  at terminals  $(a, b)$ , we suppress the 6-V source and simplify the circuit. The process leads to:

$$\mathbf{Z}_s = \mathbf{Z}_{Th} = (0.6 + j0.2) \Omega$$

For maximum power transfer:

$$\mathbf{Z}_L = \mathbf{Z}_s^* = (0.6 - j0.2) \Omega,$$

and

$$P_{av(\max)} = \frac{1}{8} \frac{|\mathbf{V}_s|^2}{R_L} = \frac{1}{8} \times \frac{(4.9)^2}{0.6} = 6.78 \text{ W.}$$